

Introduction to PLL

Ahmed Ashry

Outline


1. The need for PLL
2. PLL Specifications
3. PLL Structure
4. Type-I PLL Design
5. More PLL Types
6. Exercise (written + Matlab)

Outline (1/6)

(1) The need for PLL.

- Why PLL is needed?
- Why not simple Oscillator?
- Why not simple VCO?

Frequency selection

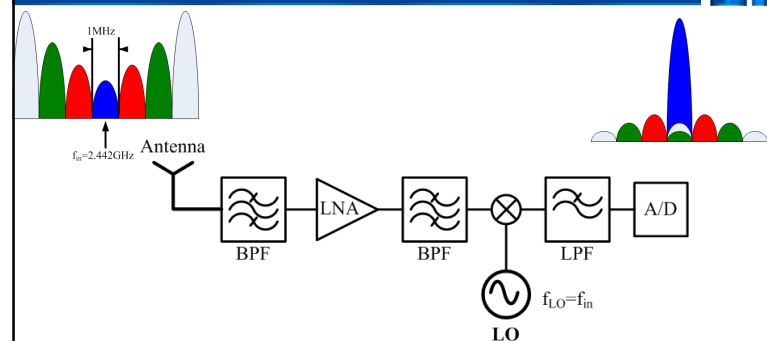

- LO frequency choose which channel to select.
- Error in LO frequency = wrong channel or more distortion

LO needed





- Very accurate.
 - Example: GSM 900MHz $\pm 0.1\text{ppm} = \pm 90\text{Hz}$
 - On-chip LC oscillator = $\pm 10\% = \pm 90\text{MHz}$
 - Crystal Oscillators (XO) are accurate, but:
 - Low Frequency $\sim 10\text{MHz}$.
 - Fixed.
- Programmable:
 - It is always needed to change the channel.
 - XOs are fixed.
 - What about VCO (Voltage Controlled Oscillator) ?


VCO is possible?



  - Ideally, VCO can be used to produce any desired frequency.
- However, practically this is impossible.




VCO is possible? No!

 

- The needed accuracy requires very stable control voltage
- Process and temperature variations make it more difficult

VCO is possible? No! (2)

 

- VCO (or generally free-running oscillator) has poor close-in phase noise compared to PLL.

Outline (2/6)




(2) PLL Specifications.

- Tuning Range
- Step Size
- Settling Time
- More.....


PLL Specifications (1)



 - Tuning Range:
 - The frequency band covered by the PLL.
 - It must cover the target application.
 - GSM: 890MHz – 915MHz




 
- Step size:
 - Must be at least equal to channel spacing.
 - GSM: 200kHz



PLL Specifications (2)



  
- Settling Time:
 - Fast switching between channels.
 - GSM: 280us (90Hz error)



PLL Specifications (3)




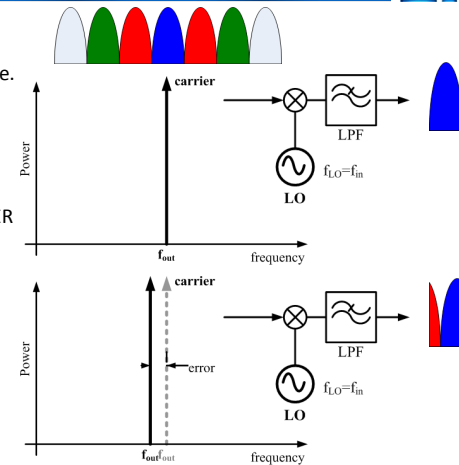- Frequency Stability:
 - Accuracy of reference source.
 - GSM: 90Hz/900MHz = 0.1ppm
 - Inaccurate frequency → wrong selection → worst BER



PLL Specifications (4)

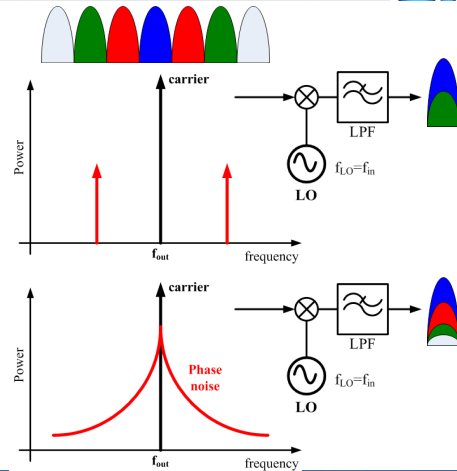- Spurs (undesired harmonics): cause interferes with other channels.
- Phase noise (random fluctuation of carrier frequency): cause interferes with other channels.



Outline (3/6)

(3) PLL Structure.

- PLL Block diagram.
- PLL Linear Model.
- PLL Main Blocks.
- PLL Simple Design.
- PLL Phase Noise

What is "Phase" ?

- It is simply the number of cycles.
- 1 cycle = 2π
- If the frequency is constant:

$$V(t) = A \cdot \sin(\omega \cdot t + \phi_o)$$


$$V(t) = A \cdot \sin(\phi(t))$$

$$\phi(t) = \omega \cdot t + \phi_o$$

- Or, generally:


$$\phi(t) = \int_0^t \omega(t) \cdot dt$$

$$\omega(t) = \frac{d}{dt} \phi(t)$$

 


PLL (Phase-Locked Loop)

 - PLL is a negative feedback system.
- It compares "Phase" not "Amplitude"
- When PLL is in lock (steady-state), feedback phase is equal to the input phase.




PLL Linear Model

 - PLL is a non-linear system.
- However, under certain conditions (near lock), it can be “linearized”.
- State variable is the phase.




PLL Blocks (1-Phase detector) 1

- XOR is the simplest PD

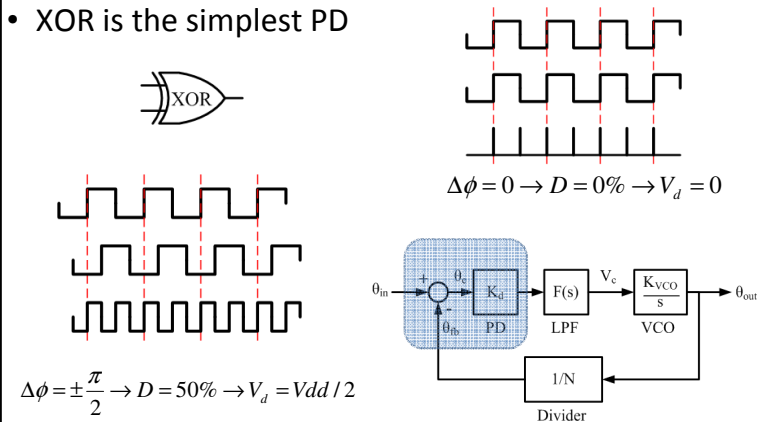


PLL Blocks (1-Phase detector) 2

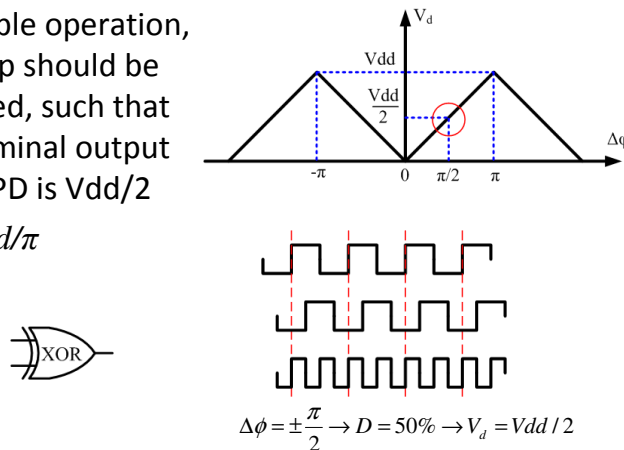- For stable operation, the loop should be designed, such that the nominal output of the PD is $V_{dd}/2$
- $K_d = V_{dd}/\pi$



PLL Blocks (2-Divider)

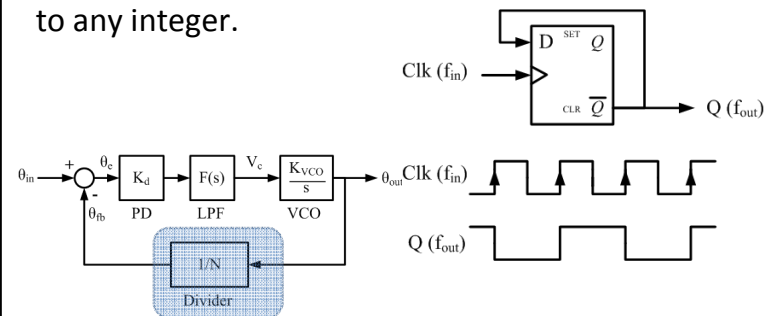
- Toggle Flip-Flop T-FF can act as a divide by 2.
- Cascading T-FFs can divide by 2^n
- Adding some logic can extend the division ratio to any integer.



PLL Blocks (3-LPF)



 - Filters the PD output.
- Weak filtering (Wide BW) leads to “Spurs”.
- Small BW leads to longer settling time.
- Filter structure determines PLL type.



PLL Blocks (4-VCO)




- VCO: **V**oltage **C**ontrolled **O**scillator.
- K_{vco} : VCO sensitivity.
- f_o : Free-running frequency.

$$\omega(t) = K_{vco} \cdot V_c$$

$$\phi(t) = \int_0^t \omega(t) \cdot dt$$

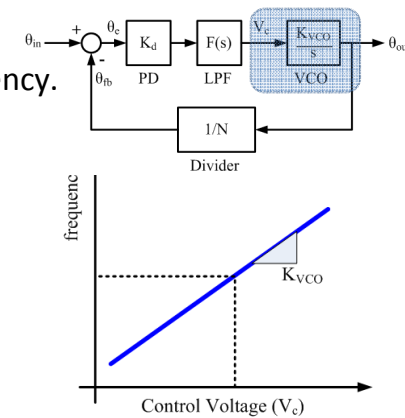
$$\phi(s) = \frac{K_{vco}}{s} \cdot V_c$$



PLL Design



 
- Given:
 - Output frequency f_{out}
 - Channel spacing. df
- Required:
 - $f_{ref} = ?$
 - $N = ?$
- Steps:
 - $f_{ref} = df$
 - $N = f_{out} / f_{ref}$



Fractional PLL



 - What if the required channel spacing is smaller than the available reference frequency?
 - Solution (1): Fractional-N PLL (out of our lecture scope)
 - Solution (2): Reference division:



Design Example



- Design a PLL for GSM ($f_{out} = 900\text{MHz}$, $df=200\text{kHz}$)
- Available reference is 13MHz.
- Solution:
 - $M=13\text{MHz}/200\text{kHz} = 65$
 - $N= 900\text{MHz}/200\text{kHz} = 4500$




Analog Dialogue

PLL Phase noise (1)



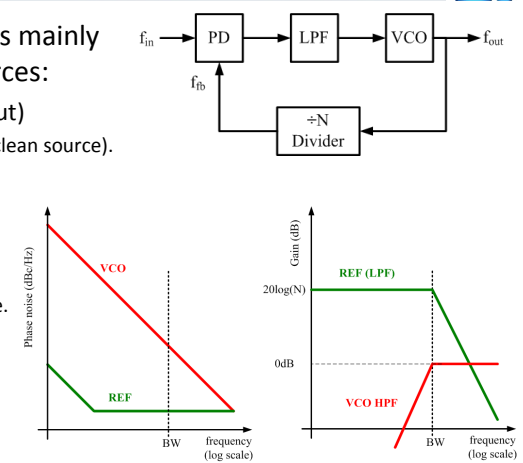
- PLL phase noise is mainly due to main sources:
 1. Reference (input)
 - Low phase noise (clean source).
 - Noise gain (N).
 - Low-pass Filter.
 2. VCO
 - Higher phase noise.
 - Unity noise gain.
 - High-pass Filter.



Phase noise (2)



 - Each noise source is shaped with the corresponding transfer function
 - Reference: Gain=N LPF. (Close-in noise)
 - VCO: Gain=1 HPF (Far-out noise)
- It is clear that (N) and (BW) determine PLL Phase Noise.



Outline (4/6)




(4) Type-I PLL.

- Type-I Design Equations.
- Design Example.

Type I PLL

 - Type I means there is only “one” integrator, which is the VCO itself.
- Very simple structure.
- Rarely used in communication systems. (Type-II is preferred)



Type I PLL

- Second order feedback system
- Open loop gain:

$$A(s) = \frac{K}{s(1+sRC)}$$

- Closed loop gain:

$$B(s) = N \frac{A(s)}{1+A(s)}$$


$$B(s) = N \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

- Natural frequency:

$$\omega_n = \sqrt{\frac{K}{RC}}$$


- Damping coefficient:

$$\xi = \frac{1}{2\sqrt{K \cdot RC}}$$

 

Zeta effect ξ

 
- Low values cause overshoot
- High values cause slow settling
- Optimum is **0.707**



BW effect $\omega_n = 2\pi \cdot f_n$

- Higher BW means fast settling.
- Settling with 5% error, Approximately:
 
$$t_s \approx \frac{4.6}{\xi \cdot \omega_n} \approx \frac{1}{f_n}$$




PLL Type-I Design (1)



- Given:
 - Output frequency f_{out}
 - Channel spacing. df
 - Settling time. t_s
 - XOR detector

- Required:

- $f_{ref}=?$
- $N=?$
- $K_o=?$

 

PLL Type-I Design (2)



Steps:

$$f_{ref} = df$$

$$N = f_{out} / f_{ref}$$


$$f_n = 1/t_s$$

$$\omega_n = 2\pi \cdot f_n \quad \xi = 0.707$$

$$RC = \frac{1}{2\xi\omega_n} \quad K = \frac{\omega_n}{2\xi}$$

- XOR detector $\rightarrow K_d = V_{dd}/\pi$

$$K_{vco} = \frac{N \cdot K}{K_d}$$

 

Exercise 1



- Design a type-I PLL with the following specifications:
 - Output center frequency 60MHz.
 - Channel spacing 1MHz.
 - Settling time 20us

Solution (1)



$$f_{ref} = df = 1\text{MHz}$$

$$N = f_{out} / f_{ref} = 60\text{MHz} / 1\text{MHz} = 60$$

$$f_n = 1/t_s = 50\text{kHz}$$

$$\omega_n = 2\pi \cdot f_n = 310\text{kr/s} \quad \xi = 0.707$$

$$RC = \frac{1}{2\xi\omega_n} = 2.3\mu\text{s} \quad K = \frac{\omega_n}{2\xi} = 220\text{kr/s}$$

$$R = 1\text{k}\Omega \quad C = 2.3\text{nF}$$

Solution (2)


- $K_d = V_{dd}/\pi = 0.38V/rad$

$$K_{vco} = \frac{N \cdot K}{K_d} = 35M(r/s)/V$$

$$K_o = \frac{K_{vco}}{2\pi} = 5.6MHz/V$$


Matlab Verification (Linear Model)

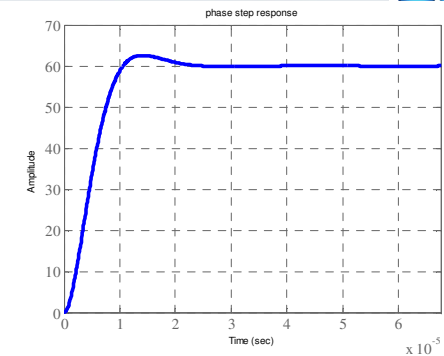- Matlab can be used to verify the linear model.




Matlab Verification (Time Model)

- Simulink Model.

 

 - Control voltage settling.
- Ripples due to reference signal.



Outline (5/6)

(5) More PLL Types.

- Type-II PLL.
- Fractional-N PLL.
- All-Digital PLL.

Type-I Limitations (1)



- Open loop gain:

$$A(s) = \frac{K}{s(1+sRC)}$$


- Phase error :

$$E(s) = \frac{1}{1+A(s)}$$

$$E(s) = \frac{s \cdot (s + 1/RC)}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

- Phase step:

$$\theta_m(s) = \frac{\Delta\phi}{s}$$

 

- Error due to phase step:

$$\theta_e(s) = \frac{(s + 1/RC) \cdot \Delta\phi}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$\theta_e(s)|_{s=0} \neq 0 \quad \theta_e(t)|_{t=\infty} \neq 0$$

- Steady-state error.

Type-I Limitations (2)



- Solution:

- Add extra pole at origin, i.e. additional integrator.
- This adds additional “s” to the equation:

$$E(s) = \frac{s^2 \cdot (s + 1/RC)}{s^2 + 2\xi\omega_n s + \omega_n^2} \quad \theta_e(s) = \frac{s(s + 1/RC) \cdot \Delta\phi}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$\theta_e(s)|_{s=0} = 0$$


$$\theta_e(t)|_{t=\infty} = 0$$

- Now, we have “2” poles at origin (Filter + VCO) → **Type-II**


Type-II Filter Implementation (1)



 - Integrator: Capacitor.
- But, with 2 poles at origin, the root-locus lies on the imaginary axis.
- The PLL is unstable (marginally).
- Filter modification is needed.




$$Z(s) = \frac{1}{s \cdot C}$$

 


Type-II Filter Implementation (2)



 - Adding extra RC section.
- Adds additional pole and zero.
- Z < P → system is conditionally stable.
- By proper design, the desired BW and damping coefficient (zeta) can be obtained.




$$Z(s) = \frac{k(s+Z)}{s \cdot (s+P)}$$

 

Type-II PFD (1)



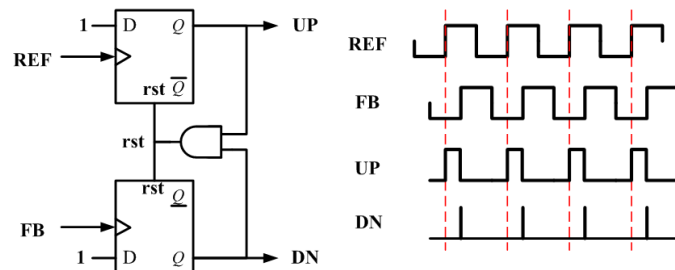
- Phase detection is usually done using PFD (Phase-Frequency Detector) “instead of XOR”



Type-II PFD (2)



 
- Better phase and frequency detection range.



Complete Type-II PLL



 - PFD:
 - Phase-Frequency Detector.
- CP:
 - Charge Pump.
- $Z(s)$:
 - Filter
- VCO:
 - Voltage-Controlled Oscillator



Outline (6/6)



(6) Exercise.

- Written part.
- Matlab part.

References



- “Introduction to Charge Pump PLL Frequency Synthesizers”, Ayman Ahmed, Si-Ware Systems.
- **National Application Note:**
<http://www.national.com/an/AN/AN-1001.pdf#page=1>
- **Fujitsu Application Note:**
<http://www.siliconrfsystems.com/Papers/U11614%20PLL%20Basics-%20Fujitsu.pdf>

Thank you

Questions?

